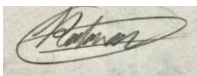


Course Title:	Electronic Circuits I
Course Number:	ELE 404
Semester/Year (e.g.F2016)	W2021

Instructor:	Fei Yuan
--------------------	-----------------

<i>Assignment/Lab Number:</i>	8
<i>Assignment/Lab Title:</i>	Amplifier Design Project

<i>Submission Date:</i>	04/18/2021
<i>Due Date:</i>	04/18/2021

Student LAST Name	Student FIRST Name	Student Number	Section	Signature*
Rahman	Taskin	500973553	11	

*By signing above you attest that you have contributed to this written lab report and confirm that all work you have contributed to this lab report is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: <http://www.ryerson.ca/senate/current/pol60.pdf>

Table of Contents

Objective.....	2
Description	2
Manual Calculations.....	3
P1	4
P2	6
P3	8
Experimental Results.....	8
E1	8
E2	9
E3	10
E4	11
Conclusion and Remarks	12

Objective

The objective of this Design Project was to build a BJT amplifier circuit that meets the following specifications:

- Power Supply: **+10V** relative to the ground;
- Quiescent current drawn from the power supply: **no larger than 10mA**;
- No-load voltage gain (at 1kHz): $|A_{vo}| = 50(\pm 10\%)$;
- Maximum no-load output voltage swing (at 1kHz): **no smaller than 8V peak to peak**;
- Loaded voltage gain (at 1kHz and with $R_L = 1k\Omega$): **no smaller than 90% of the no-load voltage gain**;
- Maximum loaded output voltage swing (at 1kHz and $R_L = 1k\Omega$): **no smaller than 4V peak to peak**;
- Input resistance (at 1kHz): **no smaller than 20k Ω** ;
- Amplifier type: **inverting or non-inverting**;
- Type of transistors: **BJT**;
- Number of transistors (stages): **no more than 3**;
- Resistances permitted: **values smaller than 220k Ω from the E24 series**;
- Capacitors permitted: **0.1 μ F, 1 μ F, 2.2 μ F, 4.7 μ F, 10 μ F, 47 μ F, 100 μ F, 220 μ F**;
- Other components (BJTs, diodes, Zener diodes etc.): **only from your ELE404 lab kit**.
- Source resistance must be 600 Ω for all tests.

Description

The configuration of the circuit I chose is a CC stage followed by CE, which is followed by another CE stage. I chose this circuit to easily achieve the desired gain of amplifier circuit that was specified. I chose the CC stage to be the first stage to meet the required input resistance. Common-collector amplifier circuits have high input resistance and low output resistance which is why I chose the CC amplifier to be

the initial stage. For the second and third stage I chose a CE amplifier to reach a high voltage gain of 50. The second stage amplified the signal by about 5. This gain was then further amplified by about 10 by the CE amplifier in the third stage with total gain being around 50. The full amplifier circuit can be found in Figure 1.

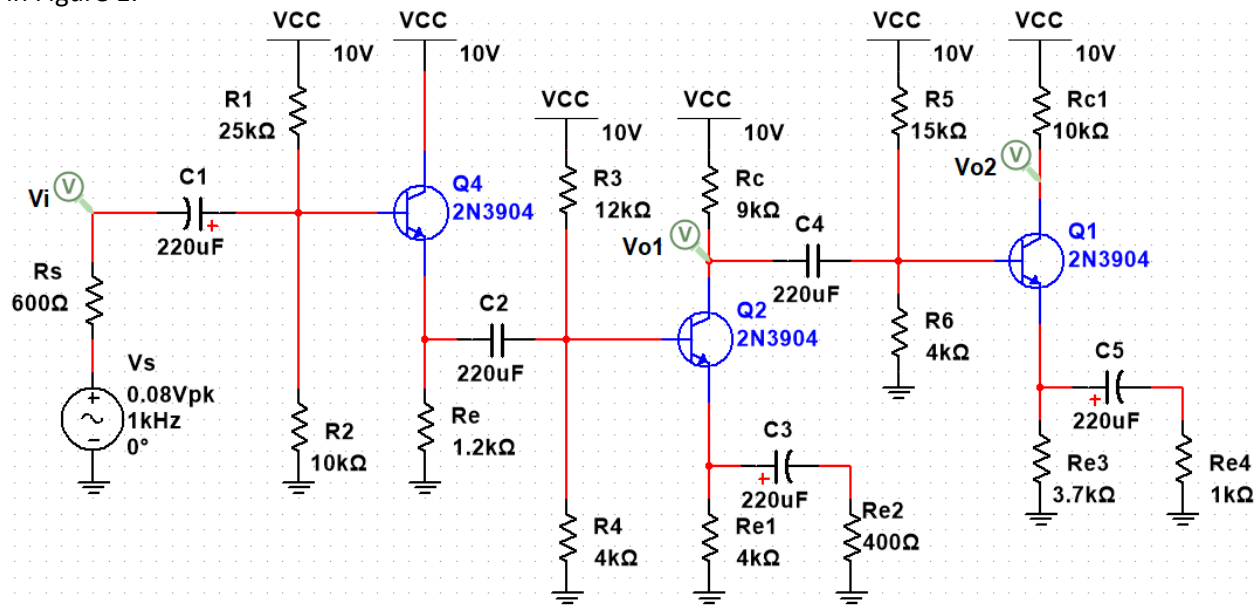


Figure 1: Complete CC-CE-CE BJT amplifier circuit.

Manual Calculations


Note: For some of the stages the values differ from the manual calculations this was done to avoid distortions in the graph.

EE404 Design Project

Tasikin Rahman
500973553


18/04/2021

1) The First Stage: CC Amplifier

 

The purpose of this amplifier circuit to attain the required input resistance. So we simply dc bias it in the active region.

Small-Signal Equivalent

 

KCL @ node V_a :

$$V_a / r_e + R_E + V_a / (R_1 || R_2) = \beta I_B + I_x$$

$$\Rightarrow V_a \left[\frac{1}{r_e + R_E} + \frac{1}{R_1 || R_2} \right] = \frac{\beta}{\beta + 1} (V_a / r_e + R_E) + I_x$$

$$\Rightarrow V_a \left[\frac{1 - \beta / (\beta + 1)}{r_e + R_E} \right] + V_a / (R_1 || R_2) = I_x \Rightarrow V_a \left[\frac{1 - \beta / (\beta + 1)}{r_e + R_E} + \frac{1}{R_1 || R_2} \right] = I_x$$

$$\Rightarrow V_a / I_x = R_{in} = \frac{1}{\left[\frac{1 - \beta}{\beta + 1} \right] \frac{1}{r_e + R_E} + \frac{1}{R_1 || R_2}}$$

$$r_e = V_T / I_E (\beta + 1) \Rightarrow V_{BE} = V_B - V_E = 0.7V$$

$$V_{BB} = V_{CC} (R_2 / (R_1 + R_2))$$

$$\Rightarrow V_{BB} - I_B R_{BB} - 0.7V - I_B (\beta + 1) R_E = 0$$

$$\Rightarrow V_{BB} - 0.7V = I_B [R_{BB} + (\beta + 1) R_E]$$

$$\Rightarrow I_B = (V_{BB} - 0.7V) / [R_{BB} + (\beta + 1) R_E]$$

If we pick resistor values in the k Ω range for R_1 and R_2 . It will no longer matter what our DC bias voltage is as it will barely change our base current. As long as we choose a DC bias voltage that is well above 0 we should have a successful CC amp.

Lets take R_1 and R_2 to be $56k\Omega$ and $45k\Omega$ respectively.

Then our base current will be :

$$V_{BB} = V_{CC} (45k\Omega / 56k\Omega + 45k\Omega) \approx 4.455V \Rightarrow R_{BB} = R_1 R_2 / (R_1 + R_2) \approx 24.95k\Omega$$

$$I_B = (V_{BB} - 0.7V) / [24.95k\Omega + (101)R_E]$$

• We want R_E to be small because when we cascade the multiple stage together the small signal equivalent circuit's eqn for I_B becomes : $I_B = (V_{BB} - 0.7V) / [R_{BB} + (101)(R_E || R_L)]$.

If R_E is small then I_B is small and so it does not affect r_e . Lets take R_E to be $1.2k\Omega$, then

$$I_B = (V_{BB} - 0.7V) / [24.95k\Omega + (101)(1.2k\Omega)] = 25.692\mu A$$

$$r_e = V_T / I_E (\beta + 1) = 10.02\Omega$$

$$R_{in} = \frac{1}{\frac{1}{r_e + R_E} + \frac{1}{R_{BB}}} = \frac{1}{\frac{1}{10.02\Omega + 1.2k\Omega} + \frac{1}{24.95k\Omega}} \approx 20.72k\Omega$$

The gain of the CC Amp :


KCL @ node V_o :

$$V_o / R_E + V_o - V_x / r_e = 0$$


$$V_o (1/R_E + 1/r_e) = V_x / r_e$$

$$\Rightarrow V_o / V_x = 1/r_e (1/R_E + 1/r_e) = 1/r_e R_E + 1$$

$$\Rightarrow V_o / V_x = R_E || r_e / r_e \approx 0.9917 \quad \therefore \text{The gain is about } 1.$$

 

P2) The Second and Third Stage :

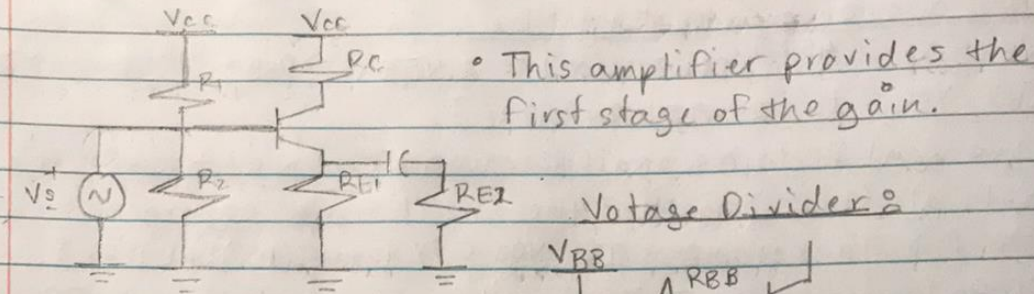

$$V_{BB} = V_{CC} (R_2 / (R_1 + R_2))$$

$$R_{BB} = R_1 \parallel R_2$$

Small Signal Equivalent :

$$R_E = R_{E1} \parallel R_{E2}$$

KCL @ node V_o :

$$V_o / R_C = -\beta I_B = \beta I_E$$

$$= \alpha \frac{V_s}{r_e + R_E} \Rightarrow V_o = -\alpha \frac{V_s R_C}{r_e + R_E}$$

No-load gain $\Rightarrow V_o / V_s = \frac{-\alpha R_C}{r_e + R_E}$

Loaded-gain :

$$\Rightarrow V_o / V_s = -\alpha (R_C \parallel R_L) / (r_e + R_E)$$

Input Resistance

$$R_{in} = V_a / I_a$$

KCL @ node V_a :

$$I_a = V_a / R_{BB} + I_E (1 - \alpha)$$

$$= V_a / R_{BB} + V_a / (r_e + R_E) (1 - \alpha)$$

$$= V_a / R_{BB} + V_a / (r_e + R_E) (1 - \beta / (B + 1)) = V_a / R_{BB} + V_a / (r_e + R_E) \cdot (1 / (B + 1))$$

$$\Rightarrow V_a / I_a = R_{in} = R_{BB} \parallel (B + 1)(r_e + R_E)$$

KVL: $V_{BB} - I_B R_{BB} - 0.7V - I_B (B+1) R_E = 0$
 $\Rightarrow V_{BB} - 0.7 / R_{BB} + (B+1) R_E = I_B$
 \Rightarrow To keep our I_B large we need a relatively small R_E in the $k\Omega$ range. Let's take $R_E = 4k\Omega$, this is necessary to properly bias the CE Amp. Let's also take relatively small R_1 and R_2 to keep our I_B large, ($R_1 = 12k\Omega$, $R_2 = 4k\Omega$) so $R_{BB} = 3k\Omega$. We need a large I_B to decrease our r_e which will increase our gain. To increase our gain during AC signal let's take a small R_{E2} relative to R_C . $R_{E2} = 400\Omega$

$$V_{BB} = 10 \left(\frac{4}{12+4} \right) = 1/4(10) = 0.4V$$

$$I_B = 3.3V / 3k\Omega + 101(4/10.4) \approx 0.08306636mA$$

$$r_e = 0.026V / 8.389702517 = 3.099\Omega$$

$$A_{v0} = -\alpha \frac{R_C}{r_e + R_E} = -\alpha \frac{R_C}{366.7\Omega} \Rightarrow A_{v1} = -\alpha \frac{(R_C || R_L)}{366.735\Omega}$$

To Avoid distortions we take $R_C = 9k\Omega$.

$A_{v0} \approx 24.2979 \Rightarrow A_{v1}$ depends on the input resistance of the Third Stage. We will calculate this gain after taking that input resistance

Input Resistance of Third Stage CE Amp:

$$R_{in} = R_{BB} || (B+1)(r_e + R_E)$$

$$R_{in} = 2.9679 || 101(15.1438\Omega + 787.23\Omega) = 2.9679 || 81.04 = 2.863k\Omega$$

$$A_{v1} \text{ of Stage 2} = -\alpha \frac{(9k\Omega || 2.863k\Omega)}{366.735\Omega} \approx -5.864$$

P3

P3) $V_{BB} = V_{CC} (R_2 / (R_1 + R_2)) \Rightarrow$ Take $R_1 = 15k\Omega$ and $R_2 = 4k\Omega$

- The dc bias resistors were chosen based on the previous stage but altered to avoid distortions
- Also, another reason why the values had to be altered

$V_{BB} \approx 2.105V$

$R_{BB} \approx 3.15789k\Omega$

$I_B = \frac{1.40526}{3.15789k\Omega + (101)0.787\Omega} \approx 16.9987\mu A$

$r_e = \frac{0.026V}{I_B(101)} \approx 15.1438\Omega$

$A_{v0} = -\frac{\alpha R_c}{r_e + R_E} = -\frac{\alpha R_c}{802.378\Omega} \Rightarrow$ Take $R_c = 9.5k\Omega$

$= -11.72258$

Full amplifier circuit ($1k\Omega$)

Experimental Results

E1

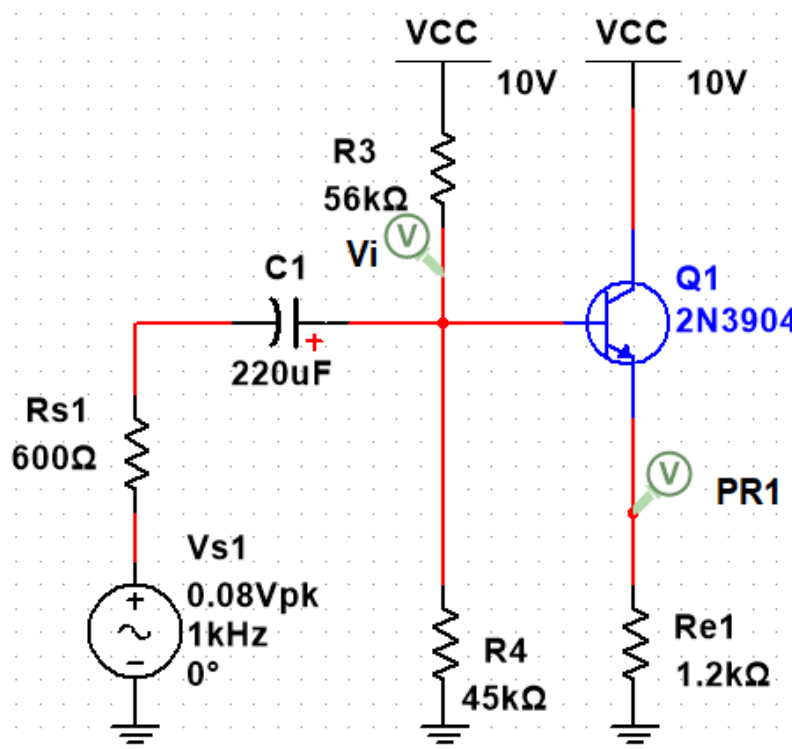


Figure 2: Stage 1 CC-Amplifier circuit.

Stage 1: CC Amplifier Graph

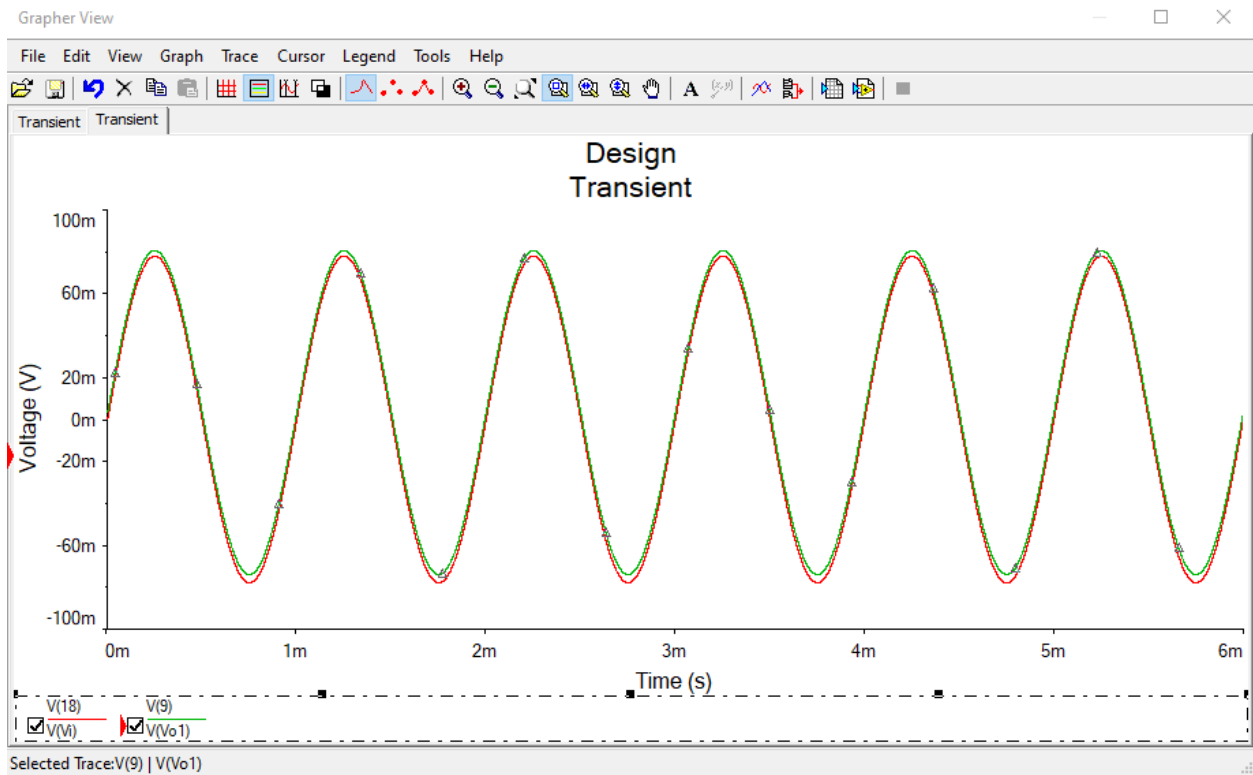


Figure 3: Input and Output voltage waveforms of stage 1 amplifier seen in Figure 2.

The manual calculations in this stage agree with the experimental results, as the gain of amplifier is about equal to 1.

E2

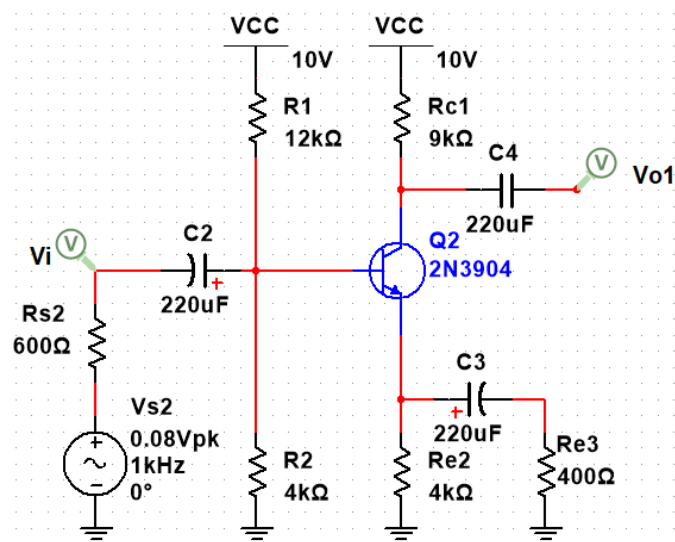


Figure 4: Stage 2 CE amplifier circuit.

Stage 2: CE Amplifier Graph

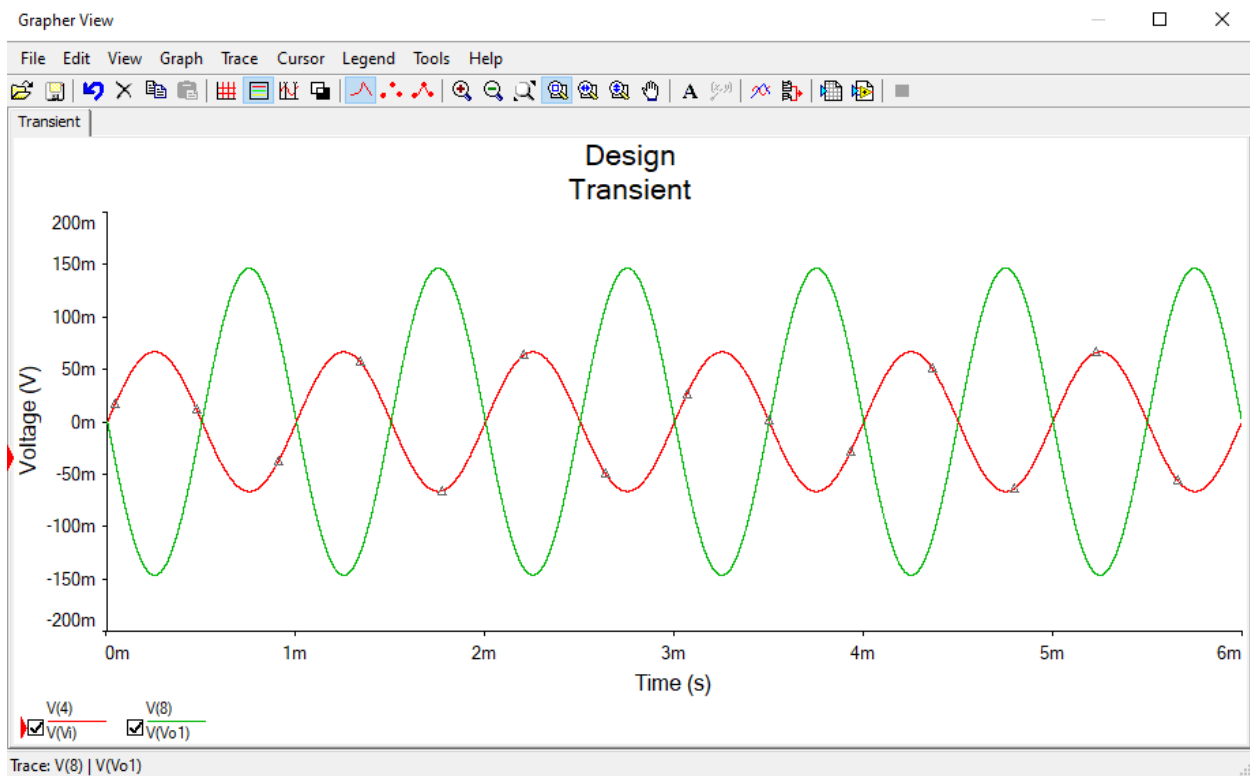


Figure 5: Input and Output waveforms of Stage 2 CE amplifier as a function of time.

E3

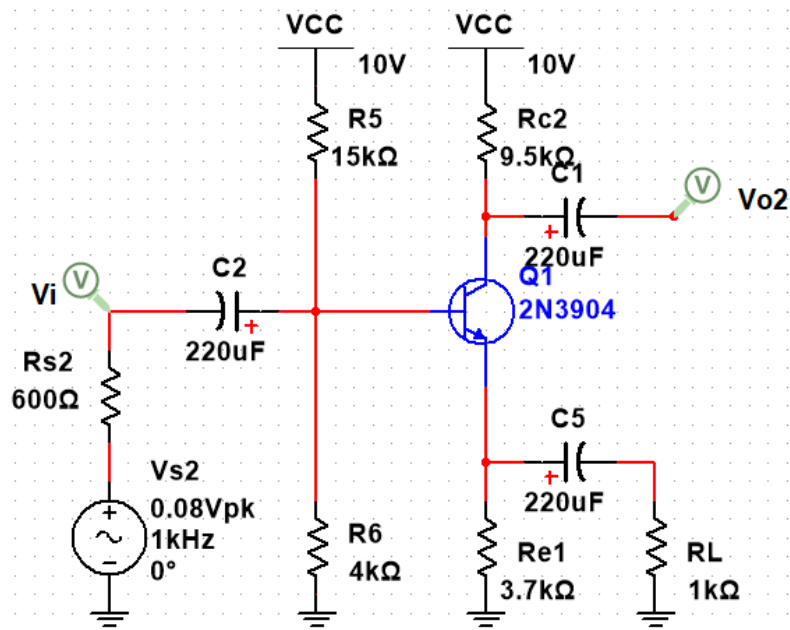


Figure 6: Stage 3 CE Amplifier circuit.

Stage 3: CE Amplifier Graph

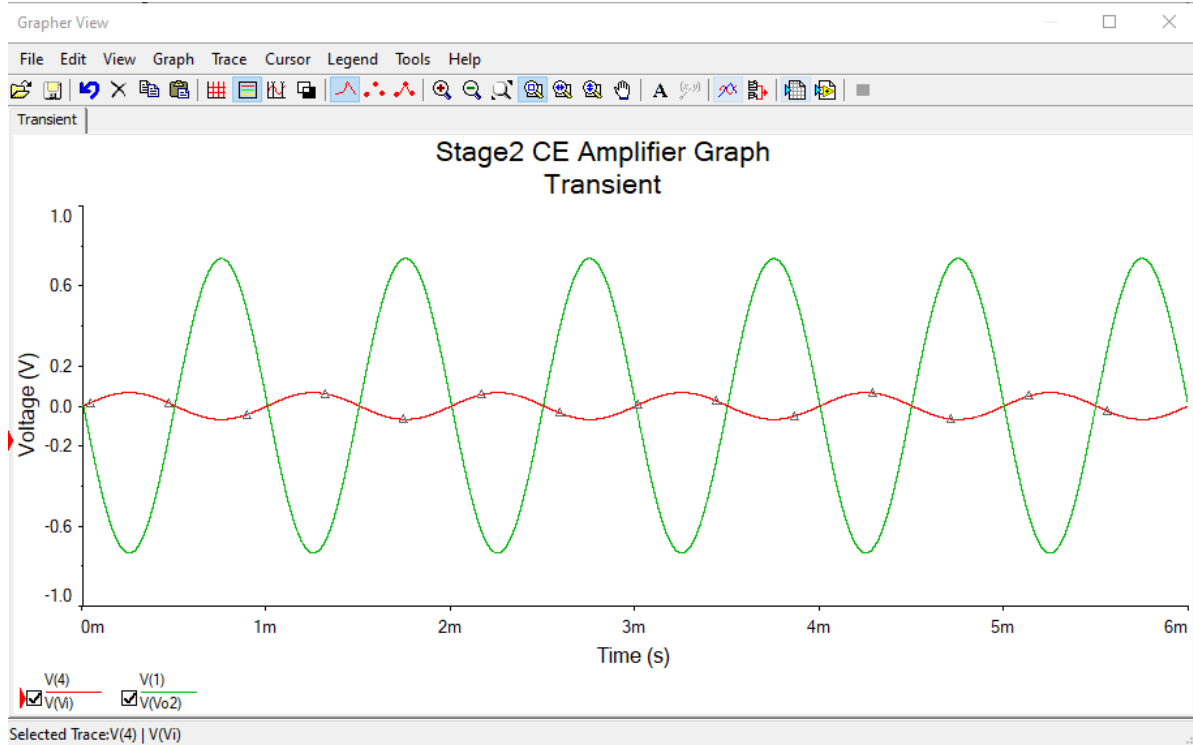


Figure 7: Input and Output waveforms of CE amplifier in Figure 6 as a function of time.

E4

Full Amplifier Circuit Graph

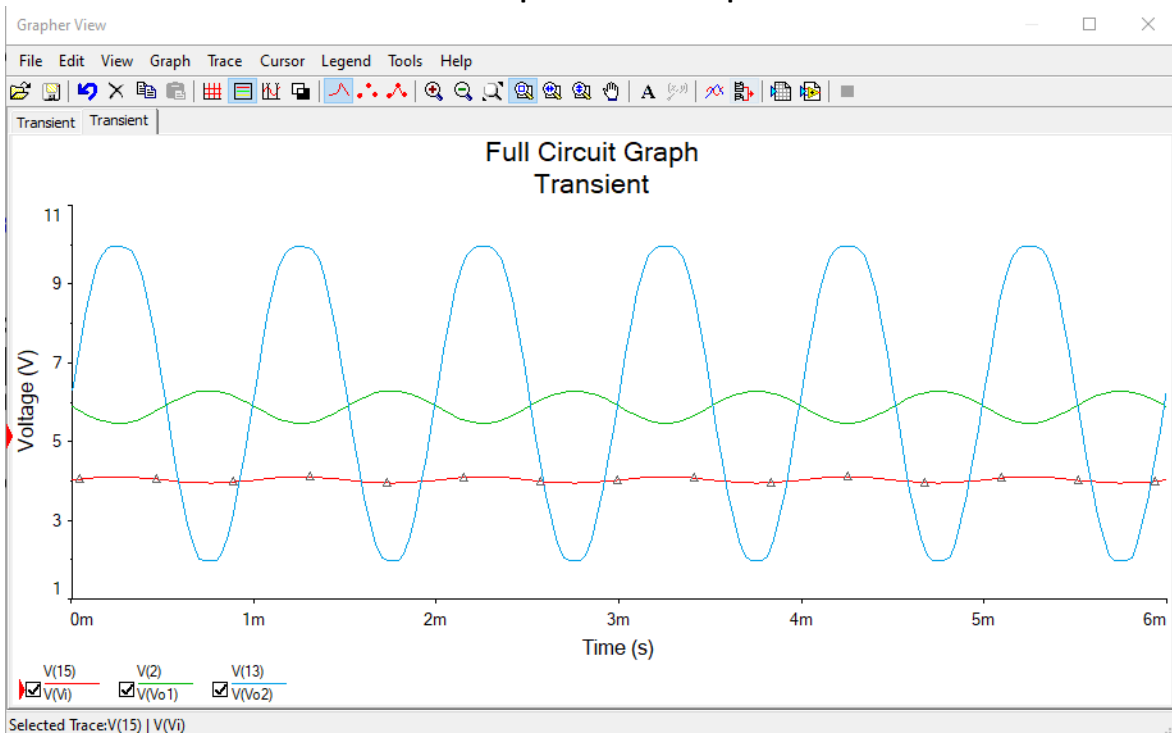


Figure 8: Input and Output waveforms of both stage2 and stage3 circuits cascaded together with stage 1, from Figure 1.

 


Figure 9: Frequency response of the amplifier circuit from 20Hz-50kHz.

Conclusion and Remarks

I can verify that the circuit meets the required standards, although there were slight discrepancies in the waveforms as the final output waveform was slightly distorted. Although the rest of the circuit seems to meet the required standards.

Compared to the manual calculation the only stage that has identical values was the first stage (CC amplifier), this is because this stage was only used to meet the required input resistance of the circuit and was not impacted by the rest of the circuit very significantly because of the emitter resistance value.

The CE amplifier in stage2 met the expected results from the manual calculations. If we look at the gain of the amplifier compared to the source waveform we see that the gain is consistent with the calculated value. The source waveform amplitude was about $77.7mV \pm 5mV$, and the output waveform of the 2nd stage amplifier was about $406mV \pm 5mV$. We can see that the amplitude increased by about 5.225, which is consistent with the calculated value of 5.864.

The CE amplifier in stage3 did not exactly meet the expected results from the manual calculations, and different resistor values were used to avoid distortions. The amplitude of the stage2 amplifier was $406mV \pm 5mV$, and the amplitude of the final output waveform was about $4V \pm 5mV$. We can see that the gain according to the experimental results was 9.8. The expected vs measured value of the gain is slightly off and this is mainly due to the minor distortion in the graph.